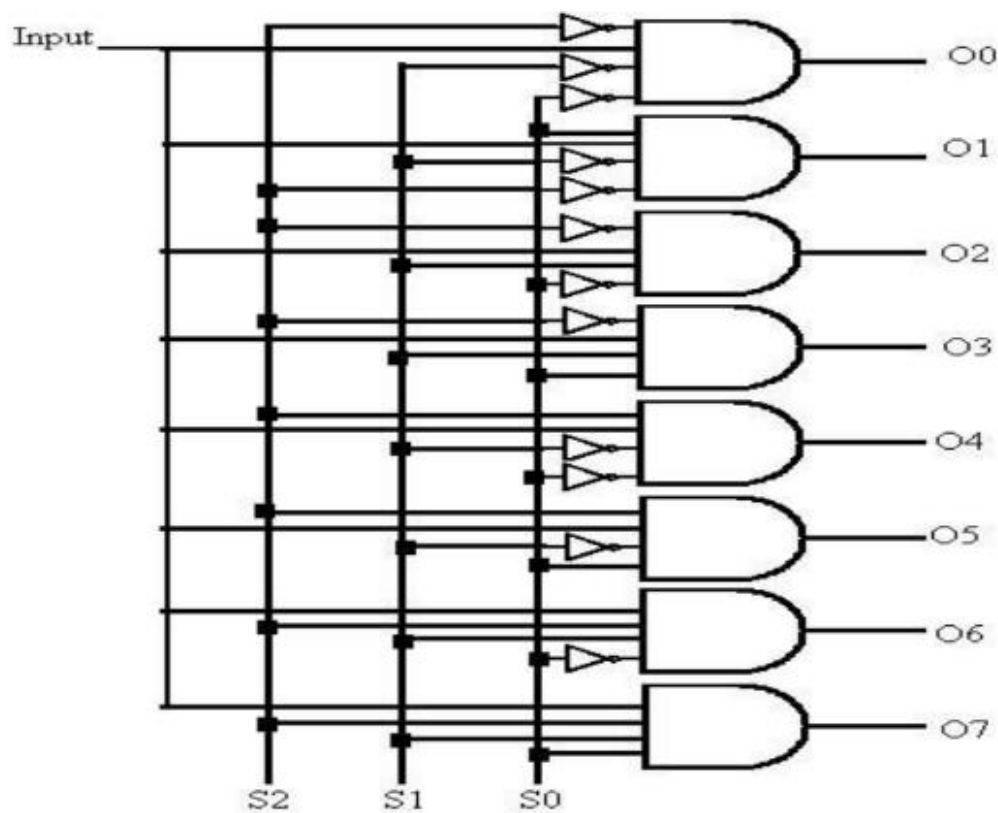


III. LEARNING ACTIVITIES

A 1:8 de multiplexer is below. You may modify your previous codes.



a. What is a demultiplexer?

A De multiplexer is a circuit that receives a single input signal and selects one of the multiple possible output routes to which to transmit the signal.

b. Create a Verilog code written in Data flow and behavioral modeling.

Data Flow Modeling

```
1 module DEMUX_1to8_DM(in,s0,s1,s2,O0,O1,O2,O3,O4,O5,O6,O7);
2 input in,s0,s1,s2;
3 output O0,O1,O2,O3,O4,O5,O6,O7;
4 assign s0n = ~ s0;
5 assign s1n = ~ s1;
6 assign s2n = ~ s2;
7 assign O0 = in & s0n & s1n & s2n;
8 assign O1 = in & s0 & s1n & s2n;
9 assign O2 = in & s0n & s1 & s2n;
10 assign O3 = in & s0 & s1 & s2n;
11 assign O4 = in & s0n & s1n & s2;
12 assign O5 = in & s0 & s1n & s2;
13 assign O6 = in & s0n & s1 & s2;
14 assign O7 = in & s0 & s1 & s2;
15 endmodule
```

Behavioral Modeling

```
1  module DEMUX_lto8_BM (in, s0,s1,s2,O0,O1,O2,O3,O4,O5,O6,O7);
2      input in, s0,s1,s2;
3      output reg O0,O1,O2,O3,O4,O5,O6,O7;
4
5      always @ (*)
6      begin
7          O0 = ~s2&in&~s1&~s0;
8          O1 = s0&in&~s1&~s2;
9          O2 = ~s2&in&s1&s0;
10         O3 = ~s2&in&s1&~s0;
11         O4 = s2&in&~s1&~s0;
12         O5 = s2&in&~s1&s0;
13         O6 = in&s2&s1&~s0;
14         O7 = in&s2&s1&s0;
15     end
```

- c. Provide a Test bench of the code.

Data Flow Modeling


```
1  module DEMUX_lto8_DM_tb;
2
3      reg in,s0,s1,s2;
4      wire O0,O1,O2,O3,O4,O5,O6,O7;
5
6      DEMUX_lto8_DM uut (
7          .in(in),
8          .s0(s0),
9          .s1(s1),
10         .s2(s2),
11         .O0(O0),
12         .O1(O1),
13         .O2(O2),
14         .O3(O3),
15         .O4(O4),
16         .O5(O5),
17         .O6(O6),
18         .O7(O7)
19     );
20     initial begin
21
22         // Initialize Inputs
23         in = 0;s0 = 0;s1 = 0;s2 = 0;
24         // Wait 100 ns for global reset to finish
25         #100;
26         // Add stimulus here
27         #100; in = 1;s0 = 0;s1 = 0;s2 = 0;
28         #100; in = 1;s0 = 1;s1 = 0;s2 = 0;
29         #100; in = 1;s0 = 0;s1 = 1;s2 = 0;
30         #100; in = 1;s0 = 1;s1 = 1;s2 = 0;
31         #100; in = 1;s0 = 0;s1 = 0;s2 = 1;
32         #100; in = 1;s0 = 1;s1 = 0;s2 = 1;
33         #100; in = 1;s0 = 0;s1 = 1;s2 = 1;
34         #100; in = 1;s0 = 1;s1 = 1;s2 = 1;
35     end
36 endmodule
37
```

Behavioral Modeling

```
1  module DEMUX_1to8_BM_tb;
2
3  reg in,s0,s1,s2;
4  wire O0,O1,O2,O3,O4,O5,O6,O7;
5
6  DEMUX_1to8_BM uut (
7  .in(in),
8  .s0(s0),
9  .s1(s1),
10 .s2(s2),
11 .O0(O0),
12 .O1(O1),
13 .O2(O2),
14 .O3(O3),
15 .O4(O4),
16 .O5(O5),
17 .O6(O6),
18 .O7(O7)
19 );
20
21 initial begin
22 // Initialize Inputs
23 in = 1;s2 = 0;s1 = 0;s0 = 0;
24 // Wait 100 ns for global reset to finish
25 #100;
26 // Add stimulus here
27 #100; s2=0; s1=0; s0=1;
28 #100; s2=0; s1=1; s0=0;
29 #100; s2=0; s1=1; s0=1;
30 #100; s2=1; s1=0; s0=0;
31 #100; s2=1; s1=0; s0=1;
32 #100; s2=1; s1=1; s0=0;
33 #100; s2=1; s1=1; s0=1;
34 end
35 endmodule
```

d. Provide simulation result of a waveform

Data Flow Modeling

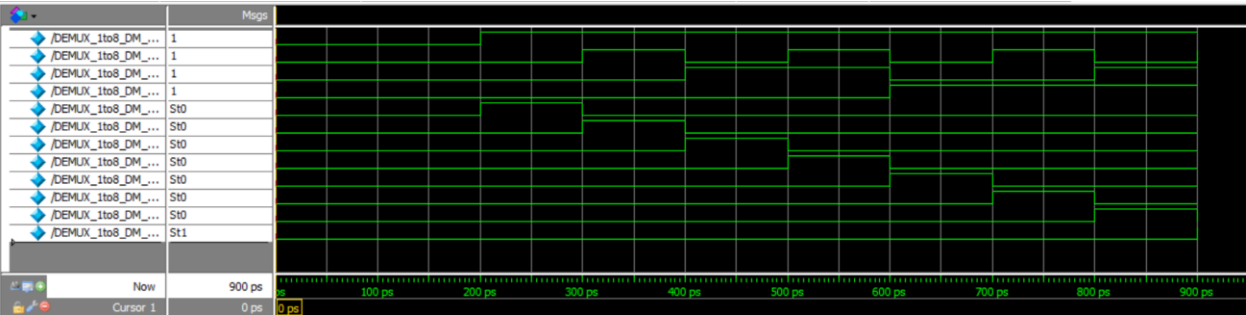

Behavioral Modeling

